


# CS 31 Homework 2: Circuits

Due at the start of class Thursday, Feb. 17, 2022

Names:

1. Fill in the truth table for the following circuit. Note that this circuit is using NOT, XOR, NOR, NAND, and AND gates.

x	y	z	$OP_1(x, y, z)$	$OP_2(x, y, z)$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

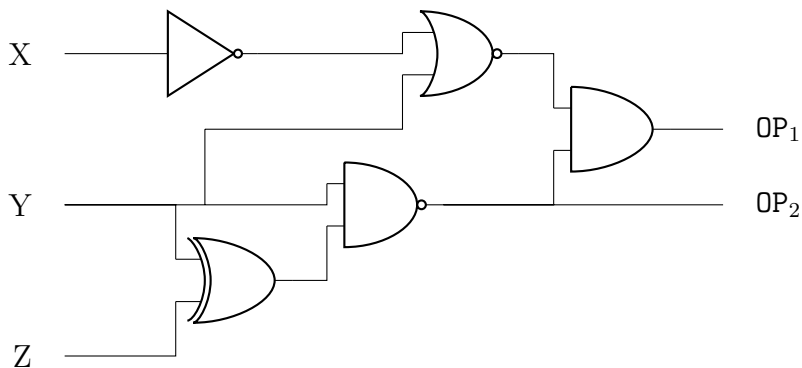

2. Construct a circuit that implements the following truth table. You may use any of the following one- or two-input gates: NOT, AND, OR, XOR, NAND, NOR, XNOR. Write out the boolean expression for OP1 and OP2 before attempting to draw the circuit. HINT: You might want to try to come up with a shorter boolean expression by considering the output values for when  $x$  is 1, and then for when  $x$  is 0.

$x$	$y$	$z$	$OP_1(x, y, z)$	$OP_2(x, y, z)$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1